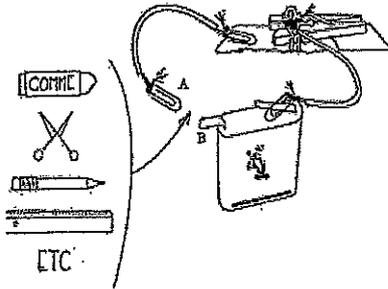




Teste différents objets en les plaçant entre la seconde languette de la pile (A) et l'extrémité libre du soquet (B) (trombone au bout du second fil).



Objet	matière	Conducteurs	Isolants	Ampoule	
				allumée	éteinte
Latte					
Trombone					
Un morceau de fil dénudé					
Un morceau de fil non dénudé					
Une gomme					
Lames des ciseaux					
Manches des ciseaux					
Un morceau de bois					
Mine de crayon					

A ton avis quelles sont les positions qui permettent d'allumer la lampe?

Diagram 1: Battery connected to the bulb, but the wire is not connected to the bulb's base. **OUI NON**

Diagram 2: Battery connected to the bulb, and the wire is connected to the bulb's base. **OUI NON**

Diagram 3: Battery connected to the wire, but the wire is not connected to the bulb. **OUI NON**

Diagram 4: Battery connected to the wire, and the wire is connected to the bulb's base. **OUI NON**

Diagram 5: Battery connected to the bulb, and the wire is connected to the bulb's base. **OUI NON**

Diagram 6: Battery connected to the wire, and the wire is connected to the bulb's base. **OUI NON**